

Alexandria University
Faculty of Engineering
Electrical Eng. Department




First Year
Electric Circuits-1
Mid-term Exam

Nov. 2017, Time Allowed: 90 Mins.

Answer All Questions

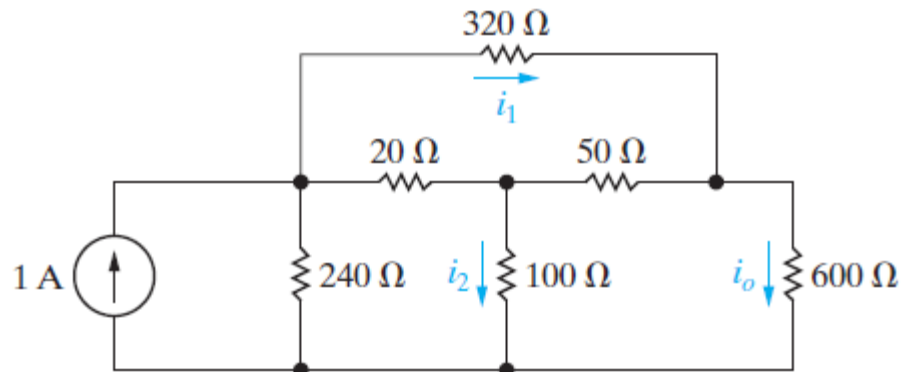
Question (1) (7 marks)

Using Y/ Δ transformation,
find the values of i_1 , i_2 , and
 i_o , and the power supplied
by the current source.



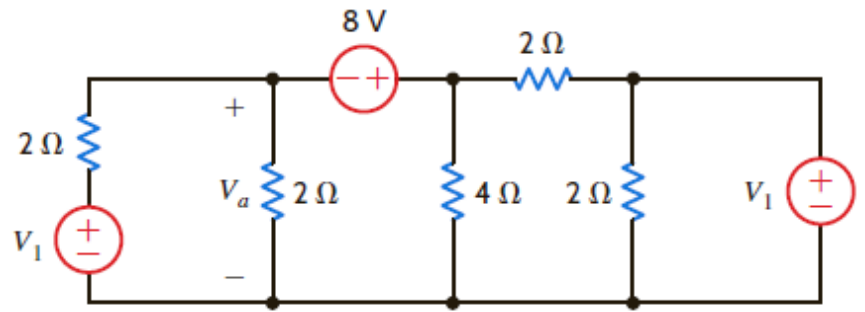
Question (2) (7 marks)

Using **KCL and KVL**,
determine the value of V_I such
that $V_a = 0$. Then check the
power balance.



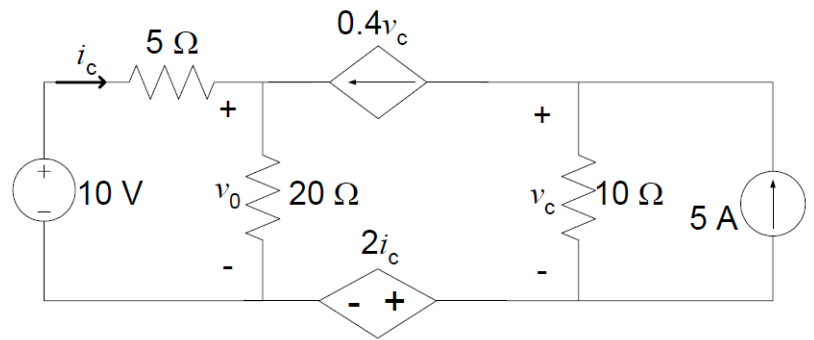Question (3) (8 marks)

Using **Superposition Theorem**,
find the power absorbed by the
 20Ω resistor.



Question (4) (8 marks)

In the circuit shown in figure, find the value of R_L for maximum power transfer, and the maximum power that can be transferred in R_L .

